

Figure 2.1: AND Gate Logic


 


Figure 2.2: AND Gate Ladder Diagram

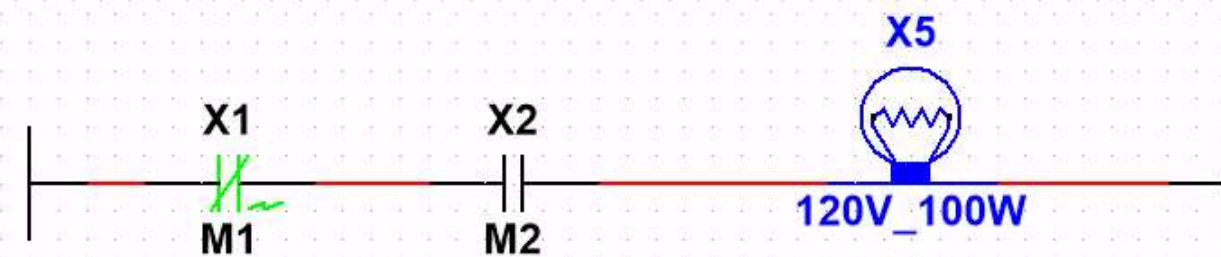


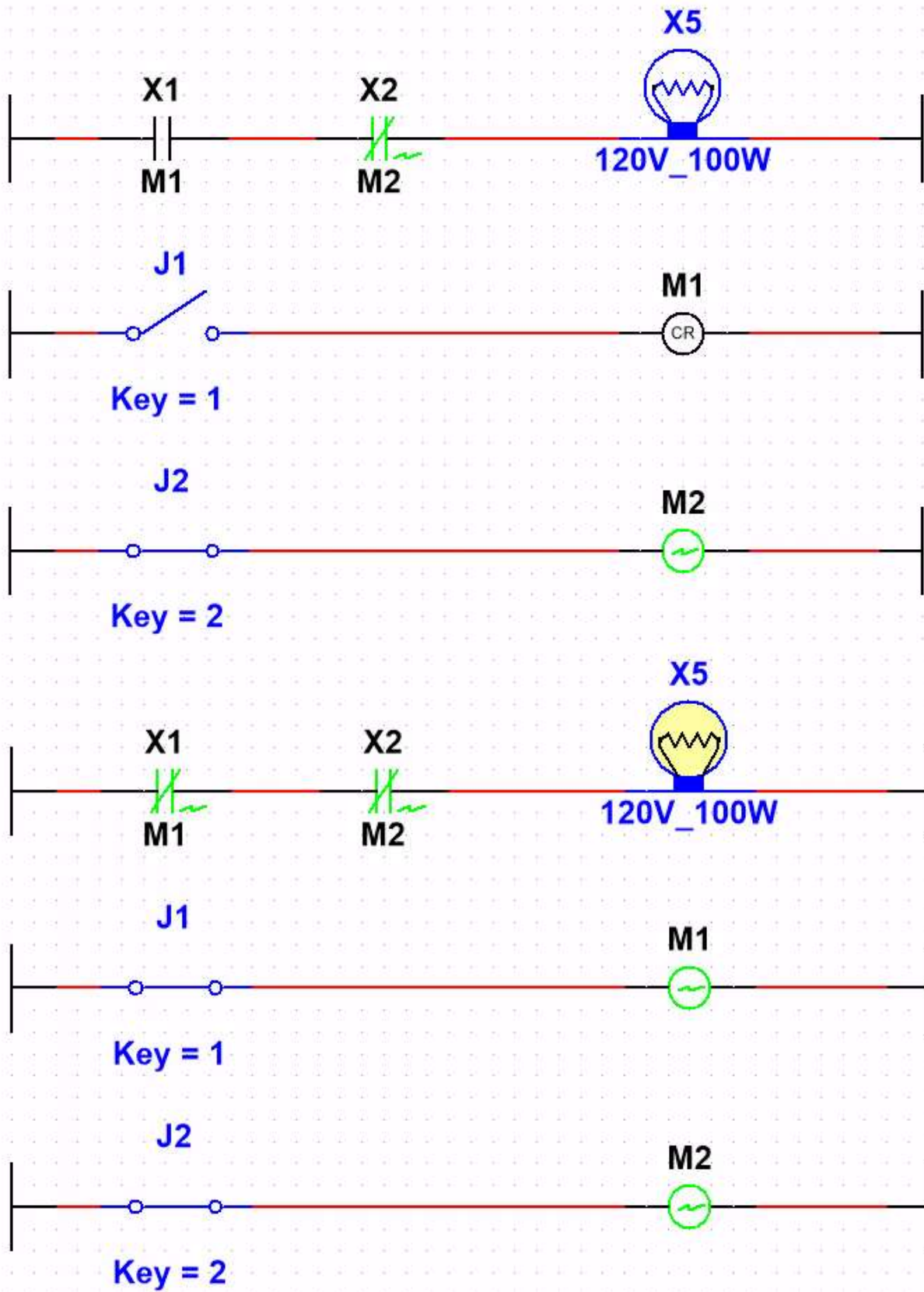


Figure 2.3: AND Gate Outputs

OR Gate

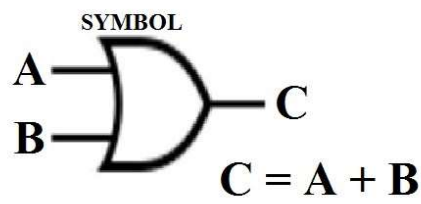

TRUTH TABLE		
INPUT		OUTPUT
A	B	A OR B
0	0	0
0	1	1
1	0	1
1	1	1

ProjectIoT123.com

Figure 2.4: OR Gate Logic


 


Figure 2.5: OR Gate Ladder Diagram

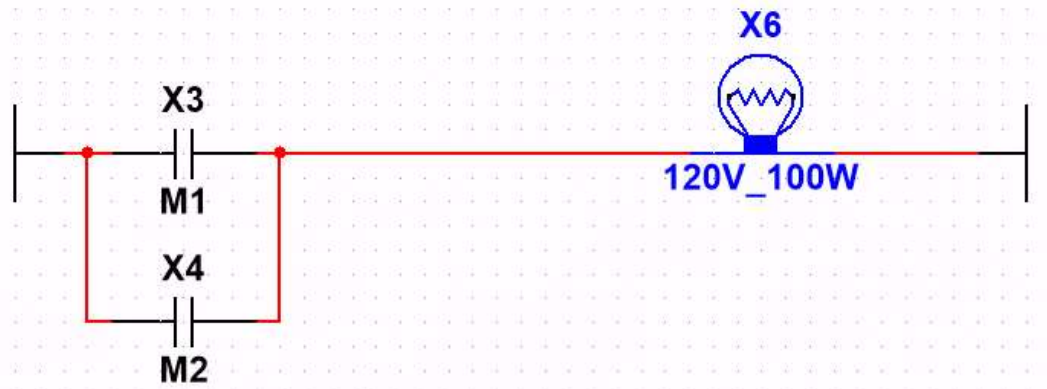


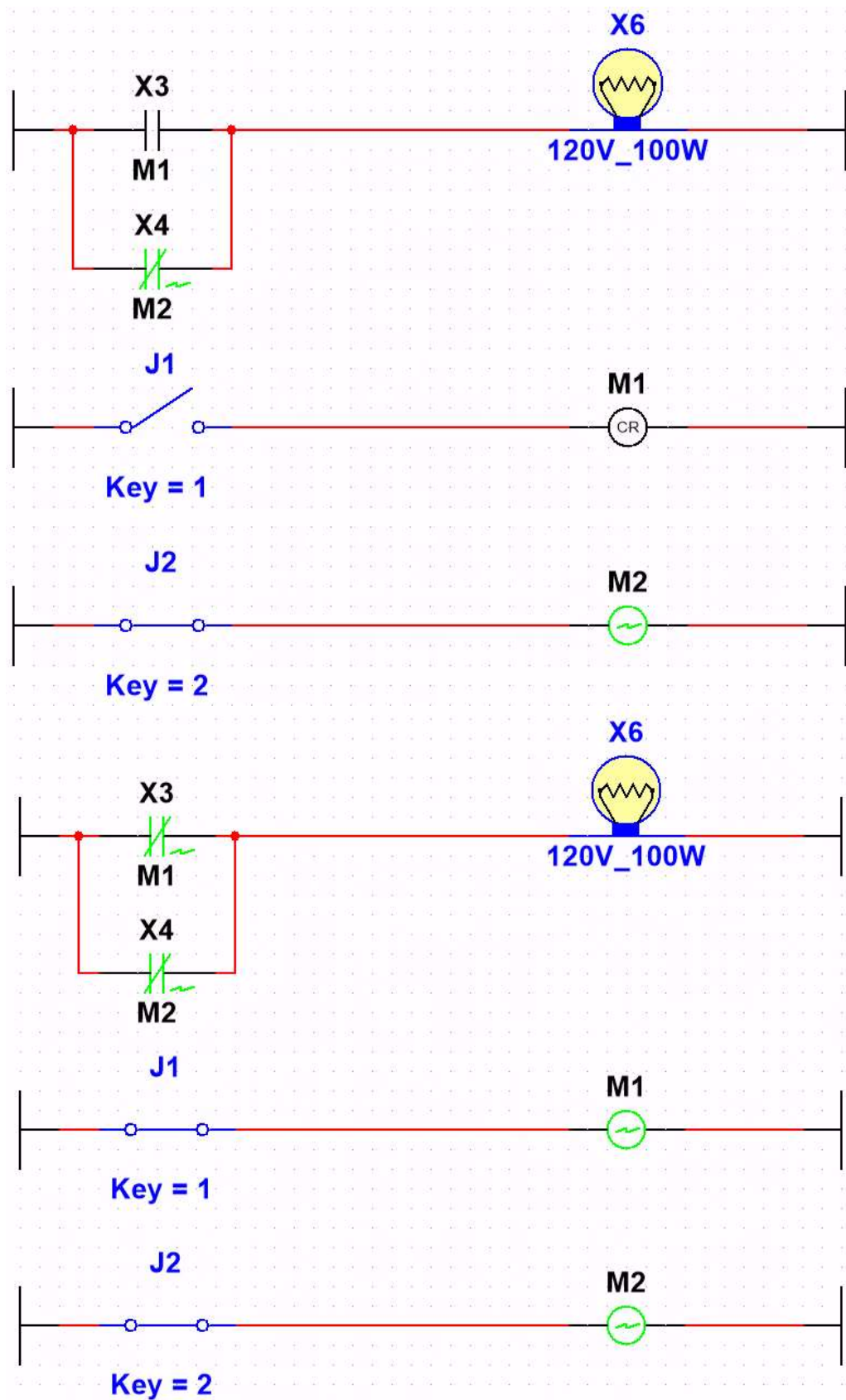


Figure 2.6: OR Gate Outputs

NAND GATE

 

Truth Table

INPUT		OUTPUT
A	B	A NAND B
0	0	1
0	1	1
1	0	1
1	1	0

ProjectIoT123.com

Figure 2.7: NAND Gate Logic


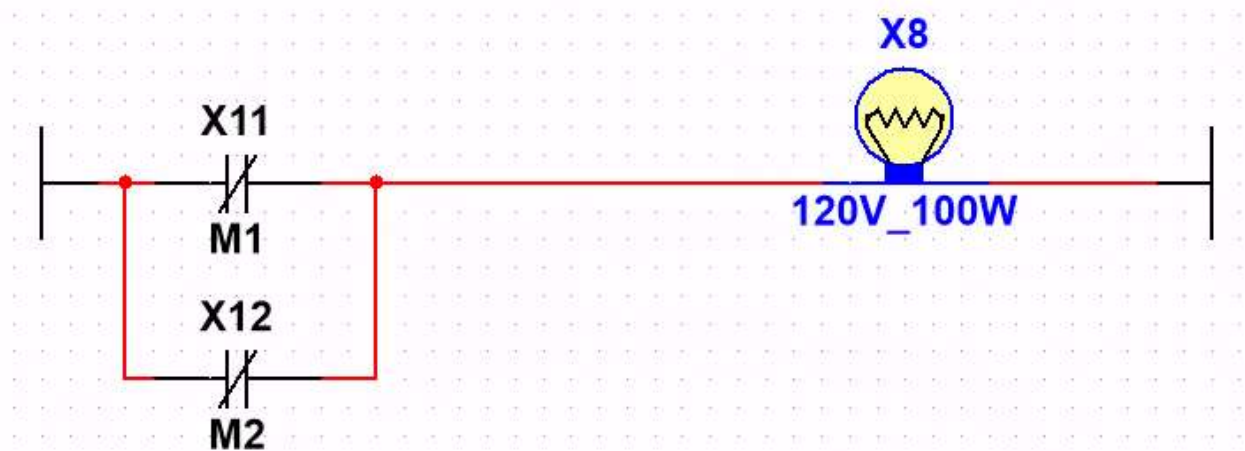


Figure 2.8: NAND Gate Ladder Diagram

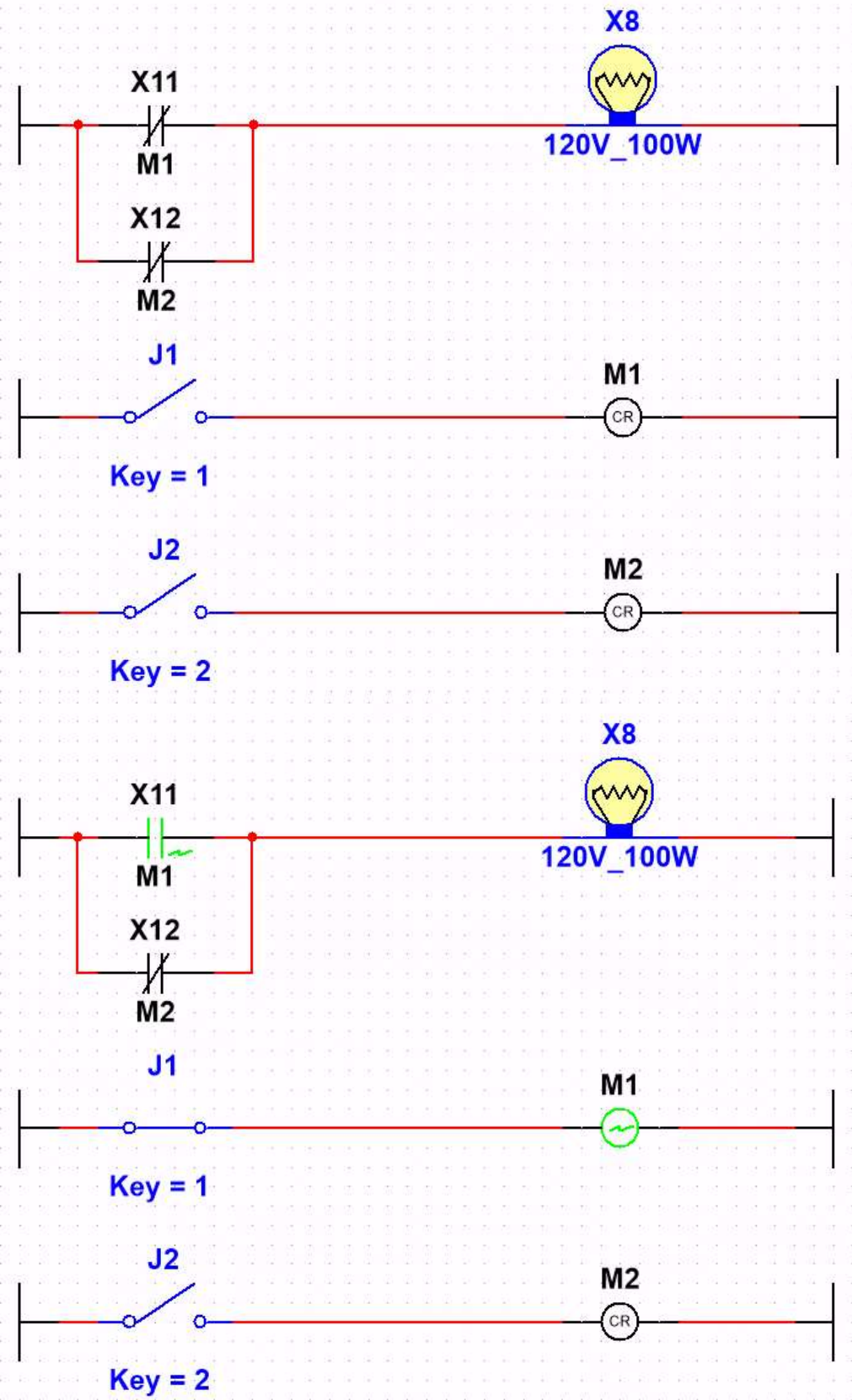


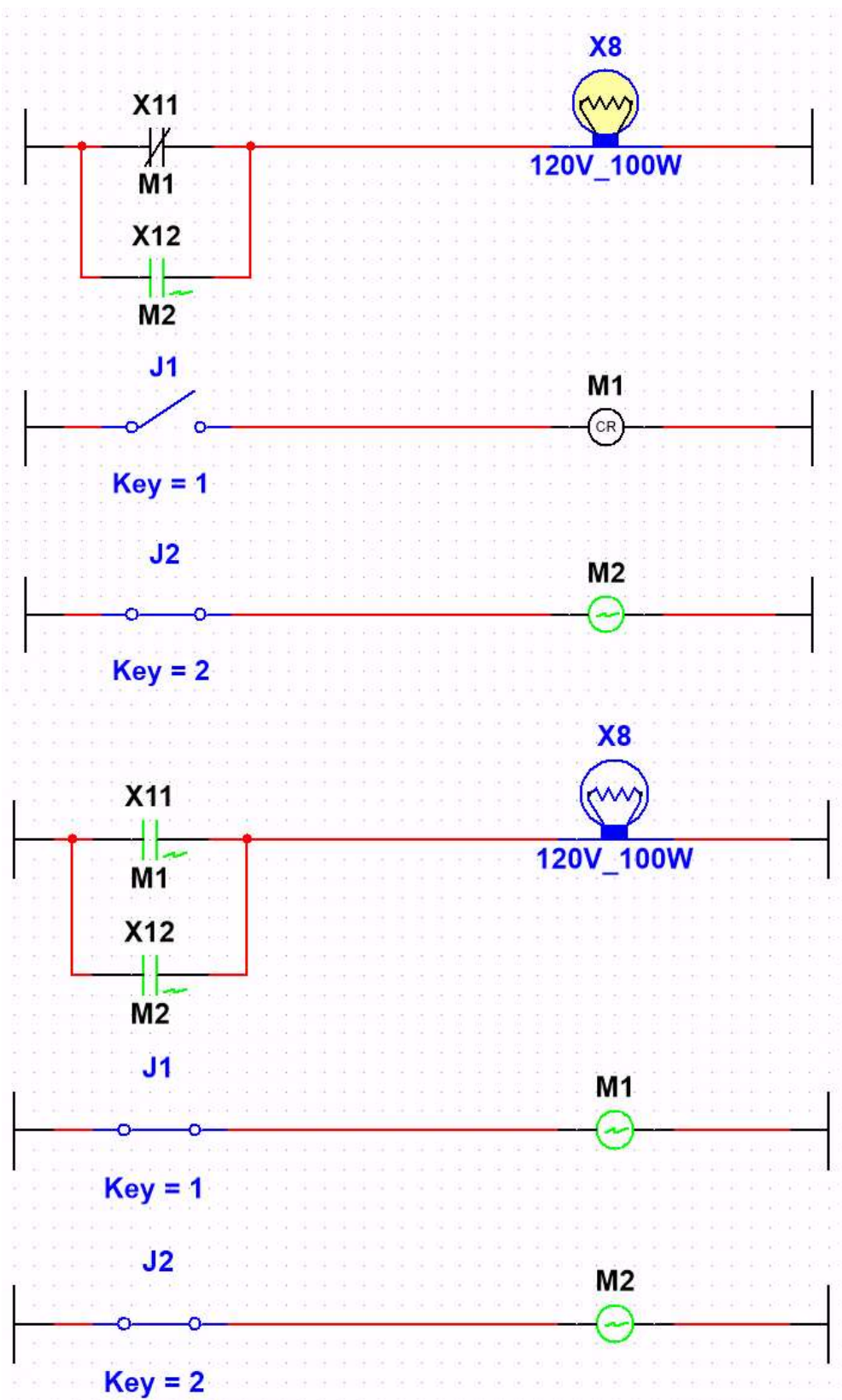


Figure 2.9: NAND Gate Outputs

NOR GATE

 

TRUTH TABLE

INPUT		OUTPUT
A	B	A NOR B
0	0	1
0	1	0
1	0	0
1	1	0

ProjectIoT123.com
Figure 2.10: NOR Gate Logic


 
 
 


Figure 2.11: NOR Gate Ladder Diagram

 

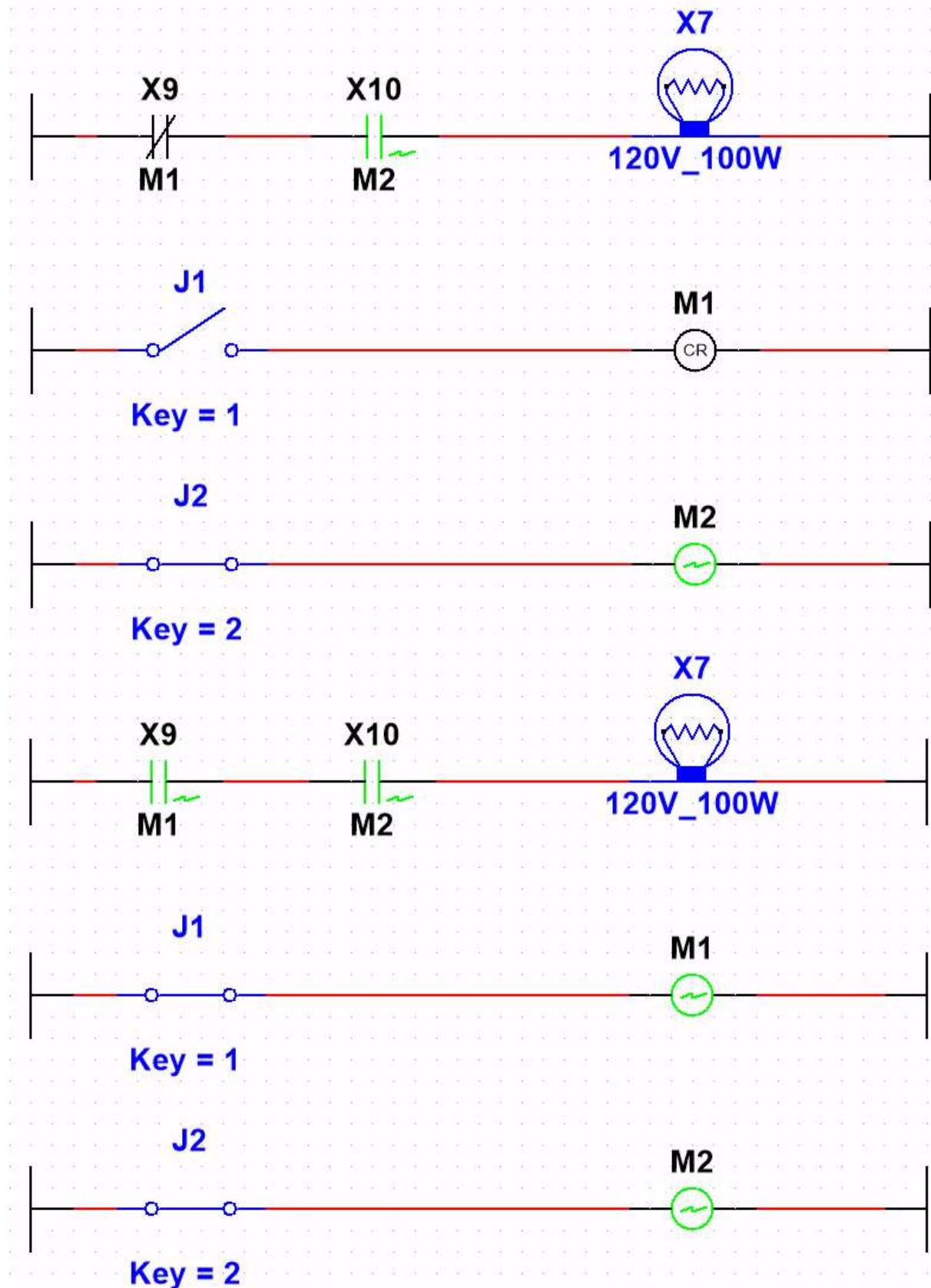


Figure 2.12: NOR Gate Outputs